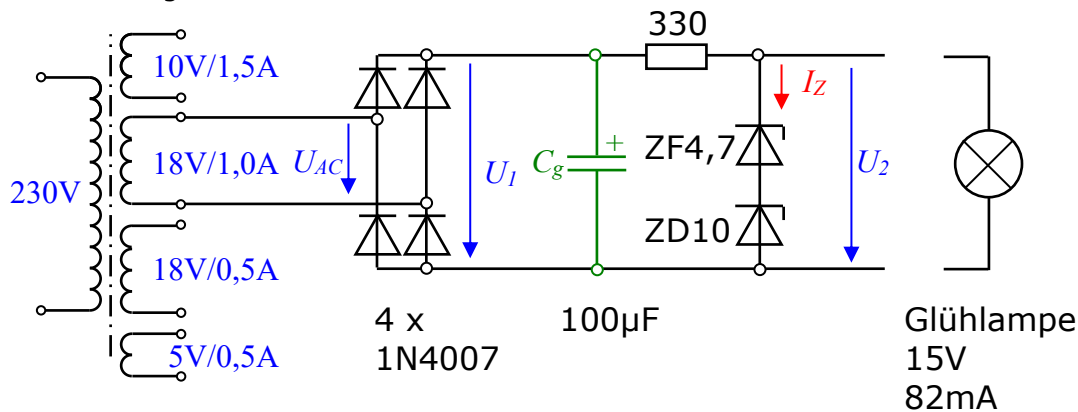


Stabilisierung einer Gleichspannung

Messung 1:

Stabilisierung mit Z-Diode



Berechnung des maximalen Diodenstromes $I_{Z\max} = \frac{P_{\text{tot}}}{U_Z} = \frac{500\text{mW}}{15\text{V}} = \frac{0,5\text{W}}{15\text{V}} = 0,033\text{A}$ (der gewählte Wert muss darunter liegen!)

Berechnung des minimalen Diodenstromes $I_{Z\min} = I_{Z\max} \cdot 0,1 = 0,0033\text{A}$ (10% von $I_{Z\max}$)

Berechnung des Vorwiderstandes $R_V = \frac{U_1 - U_Z}{I_Z} = \frac{20,1\text{V} - 16\text{V}}{15\text{mA}} = \frac{4,1\text{V}}{0,015\text{A}} = 273,3\Omega$

(gewählt $R_V = 330\Omega$)

Philips Semiconductors

Product specification

Voltage regulator diodes

BZX55 series

FEATURES

- Total power dissipation: max. 500 mW
- Tolerance series: $\pm 5\%$
- Working voltage range: nom. 2.4 to 75 V (E24 range)
- Non-repetitive peak reverse power dissipation: max. 40 W.

DESCRIPTION

Low-power voltage regulator diodes in hermetically sealed leaded glass SOD27 (DO-35) packages.
The diodes are available in the normalized E24 $\pm 5\%$ tolerance range. The series consists of 37 types with nominal working voltages from 2.4 to 75 V (BZX55-C2V4 to BZX55-C75).

APPLICATIONS

- Low voltage stabilizers or voltage references.



The diodes are type branded.

Fig.1 Simplified outline (SOD27; DO-35) and symbol.

LIMITING VALUES


In accordance with the Absolute Maximum Rating System (IEC 134).

SYMBOL	PARAMETER	CONDITIONS	MIN.	MAX.	UNIT
I_F	continuous forward current		–	250	mA
I_{ZSM}	non-repetitive peak reverse current	$t_p = 100\text{ }\mu\text{s}$; square wave; $T_j = 25\text{ }^\circ\text{C}$ prior to surge	see Table "Per type"		
P_{tot}	total power dissipation	$T_{\text{amb}} = 50\text{ }^\circ\text{C}$; note 1	–	400	mW
		$T_{\text{amb}} = 50\text{ }^\circ\text{C}$; note 2	–	500	mW
P_{ZSM}	non-repetitive peak reverse power dissipation	$t_p = 100\text{ }\mu\text{s}$; square wave; $T_j = 25\text{ }^\circ\text{C}$ prior to surge	–	40	W
		$t_p = 8.3\text{ ms}$; square wave; $T_j \leq 150\text{ }^\circ\text{C}$ prior to surge	–	30	W
T_{stg}	storage temperature		–65	+200	$^\circ\text{C}$
T_j	junction temperature		–	200	$^\circ\text{C}$

Notes


1. Device mounted on a printed circuit-board without metallization pad; lead length max.
2. Tie-point temperature $\leq 50\text{ }^\circ\text{C}$; lead length 8 mm.

Ergebnis:

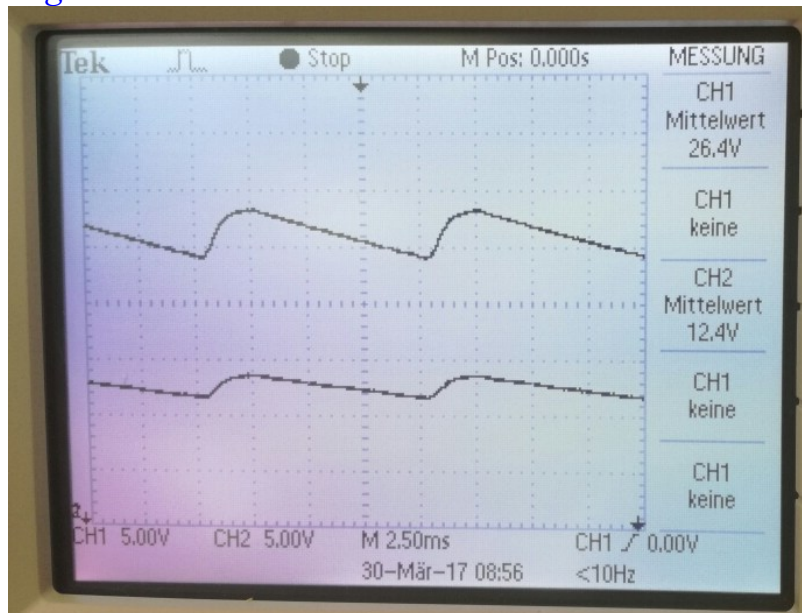

Messung 2:

Stabilisierung mit Längstristor

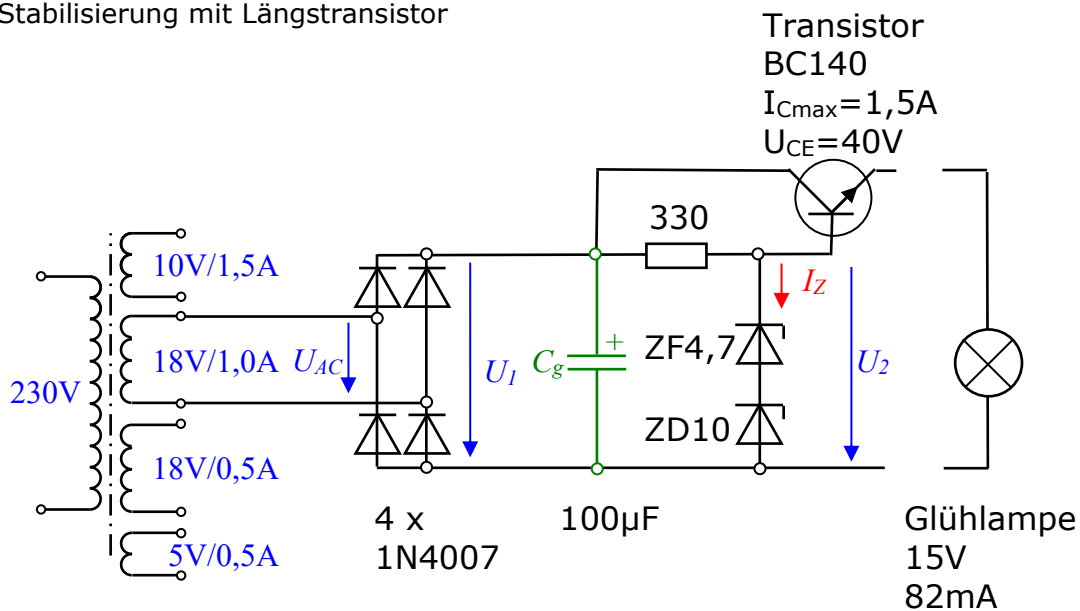

Philips Semiconductors

Product specification

NPN medium power transistors

BC140; BC141

FEATURES

- High current (max. 1 A)
- Low voltage (max. 60 V).

APPLICATIONS

- General purpose switching and amplification.

DESCRIPTION

NPN medium power transistor in a TO-39 metal package. PNP complements: BC160 and BC161.

PINNING

PIN	DESCRIPTION
1	emitter
2	base
3	collector, connected to case


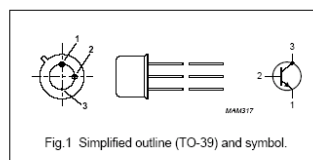


Fig.1 Simplified outline (TO-39) and symbol.

QUICK REFERENCE DATA

SYMBOL	PARAMETER	CONDITIONS	MIN.	TYP.	MAX.	UNIT
V_{CB0}	collector-base voltage	open emitter	—	—	80	V
	BC140		—	—	100	V
	BC141		—	—	100	V
V_{CE0}	collector-emitter voltage	open base	—	—	40	V
	BC140		—	—	60	V
	BC141		—	—	60	V
I_{CM}	peak collector current		—	—	1.5	A
P_{tot}	total power dissipation	$T_{case} \leq 45^\circ C$	—	—	3.7	W
h_{FE}	DC current gain	$I_C = 100 \text{ mA}; V_{CE} = 1 \text{ V}$	63	100	160	
	BC140-10; BC141-10		100	160	250	
	BC140-16; BC141-16		100	160	250	
f_T	transition frequency	$I_C = 50 \text{ mA}; V_{CE} = 10 \text{ V}; f = 100 \text{ MHz}$	50	—	—	MHz

Ergebnis

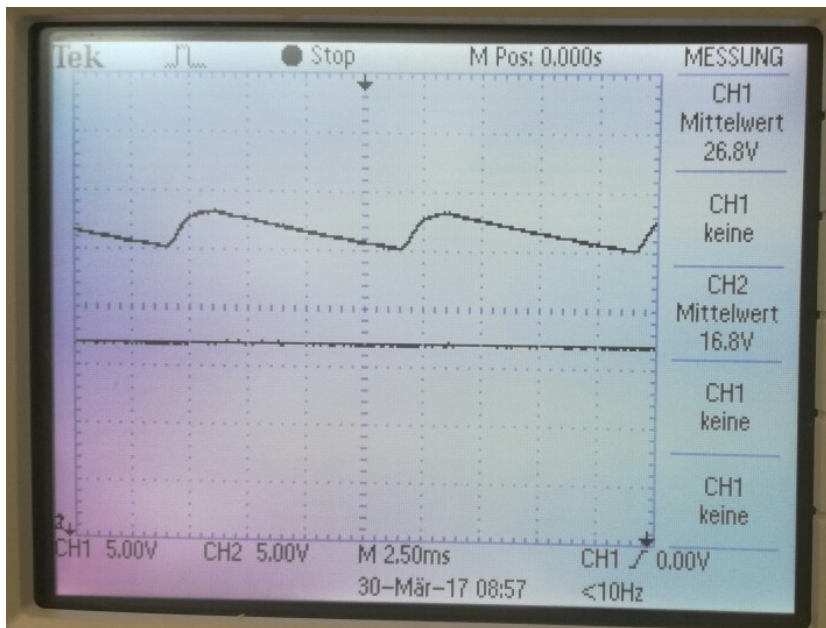

Berechnung der Schaltung

1) Gleichrichterberechnung

$$\hat{U} = \sqrt{2} \cdot U_{eff} = 1,4 \cdot 18V = 25,2V$$

Die gewünschte Gleichspannung soll 15V betragen. $\leftarrow U_2$

Das heißt: Die Brummspannung darf maximal $U_{Br} = \hat{U} - U_2$ sein.

$$U_{Br} = \hat{U} - U_2 = 25,2V - 15V = 10,2V$$

Damit haben wir aber keine Reserven mehr, deshalb wählen wir für die Eingangsspannung

$$U_1 = \hat{U} - \frac{U_{Br}}{2} = 25,2V - 5,1V = 20,1V$$

2) Berechnung der Zenerdioden-Stabilisierung

$$U_Z = 0,7V + U_2 = 0,7V + 15V \approx 16V$$

$$I_{Z\max} = \frac{P_{tot}}{U_Z} = \frac{500mW}{15V} = \frac{0,5W}{15V} = 0,033A \quad (\text{der gewählte Wert muss darunter liegen!})$$

$$R_V = \frac{U_1 - U_Z}{I_Z} = \frac{20,1V - 16V}{30mA} = \frac{4,1V}{0,03A} = 136,7\Omega \quad (\text{gewählt } R_V = 150\Omega)$$

3) Berechnung des Glättungskondensators

$$C = \frac{I_L}{U_{Br}} \cdot 1,8 = \frac{1500mA}{5V} \cdot 1,8 = 540\mu F$$

$$I_L \hat{=} I_{C\max}$$

$$(\text{gewählt } C_g = 470\mu F)$$

4) *Berechnung der Belastung*

$$R_{L\min} = \frac{U_2}{I_{c\max}} = \frac{15V}{1,5A} = 10\Omega$$

$$P_V = U_2 \cdot I_L = 15V \cdot 1,5A = 22,5W$$

5) *Berechnung des Transistors*

$$I_B = \frac{I_C}{B} = \frac{1,5A}{100} = 15mA$$

$$U_{1\max} = \frac{P_{TOT} + P_L}{I_L} = \frac{3,7W + 15V \cdot 0,5A}{0,5A} = 22,4V .$$

$$I_{1\max} = \frac{P_{TOT}}{U_1 - U_2} = \frac{3,7W}{20,1V - 15V} = 0,73A$$